

# Design Review

FLASH ADC



UNIVERSIDAD TECNICA  
FEDERICO SANTA MARIA

Alan Rivera  
15-12-2023




The background of the slide is a dark blue, high-contrast image of a printed circuit board (PCB). The intricate patterns of the circuit traces, pads, and vias are visible, creating a complex geometric texture. The word "Especificaciones" is centered in a clean, white, sans-serif font, standing out prominently against the dark, technical background.

# Especificaciones


# Referencias:

- Flash ADC Behzad Razavi
- <https://www.electronics-tutorial.net/analog-integrated-circuits/data-converters/flash-type-adc/>
- <https://www.semanticscholar.org/paper/Low-Power-and-High-Speed-CMOS-Comparator-for-A-D-A-Kumari-Kumar/7074d7ad974dc4933a87081948ba5e3980702a64>

# Flash ADC

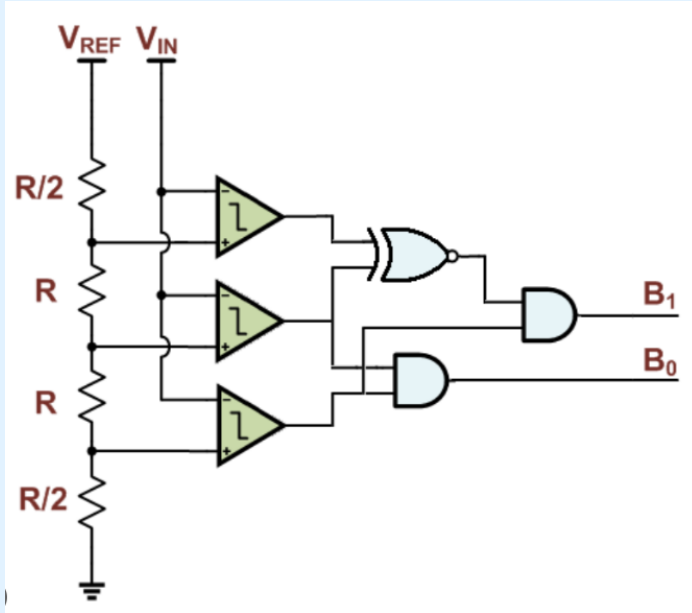


# Comparador

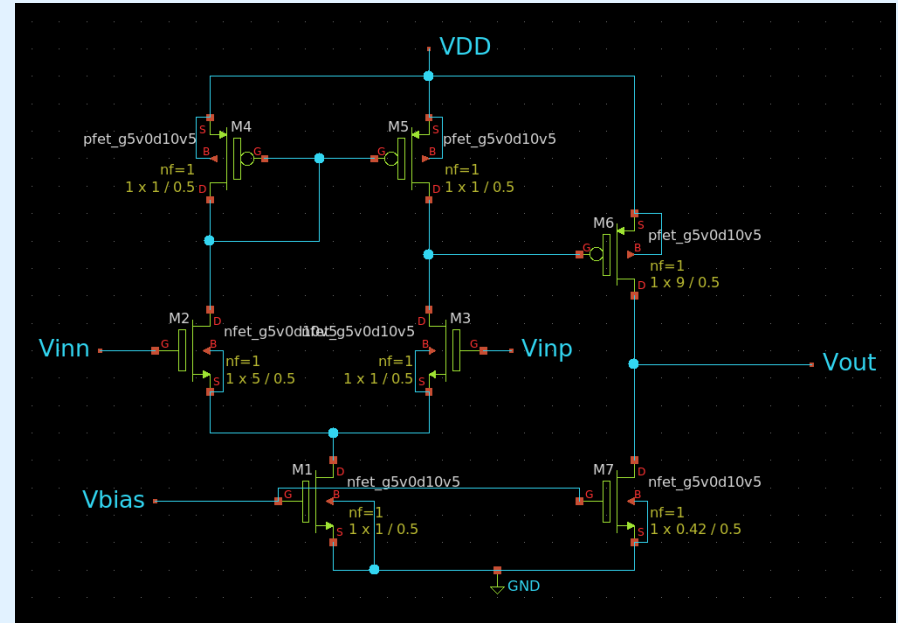


# Codificador

- Inversor.

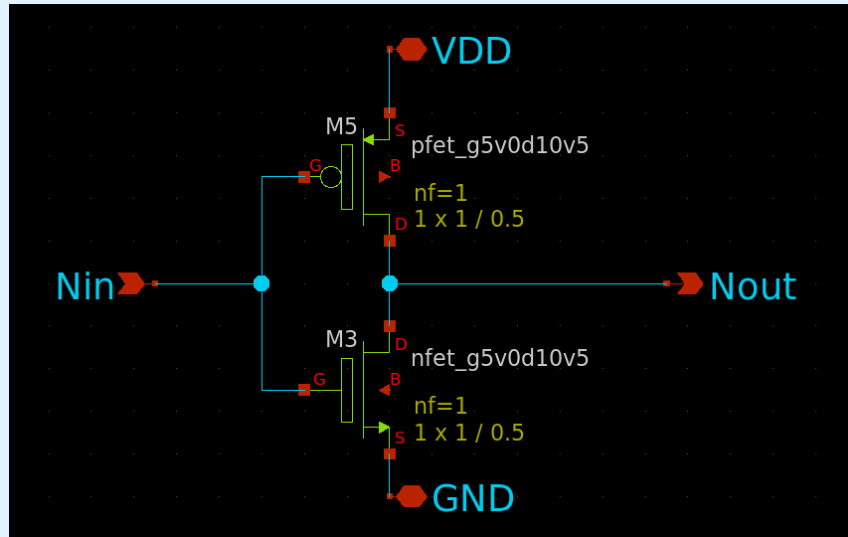

- Nand.

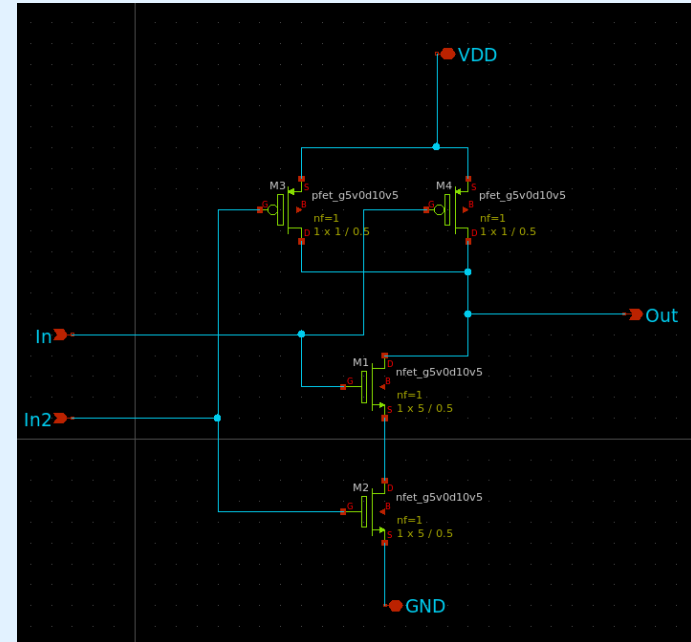

# Sensor infrarrojo – Señal Analógica

- Sensor de Proximidad Infrarrojo IR Modelo E18-D80NK Versión S
- 5V

Sensor → Comparadores → Codificador → Bits

# Especificaciones


Señal del sensor	0v – 5v
Transistores	5v
VDD	5v
Vref	5v



A detailed, high-magnification image of a microchip, showing a complex grid of various colored squares and rectangles in shades of green, blue, yellow, and brown. The pattern is dense and irregular, representing the intricate circuitry of a semiconductor device. The word "Simulación" is centered over this background.


Simulación



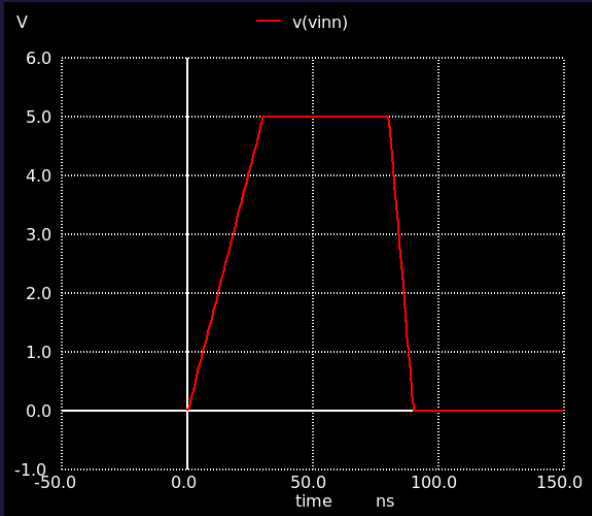

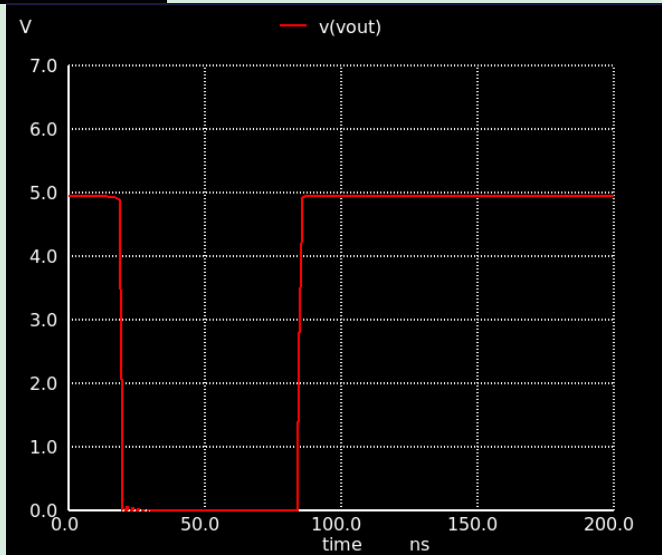
## Comparador:


- $V_{ref} = 3V$
- $V_{bias} = 1V$
- Transistores genéricos.
- Señal variable.



- $V_{ref} = 0.5$
- $V_{ref} = 4.5$

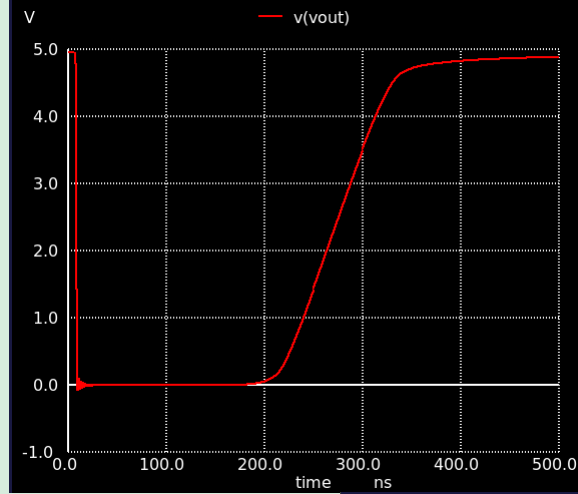


- $V_{bias}$ .
- Tamaño de transistores.


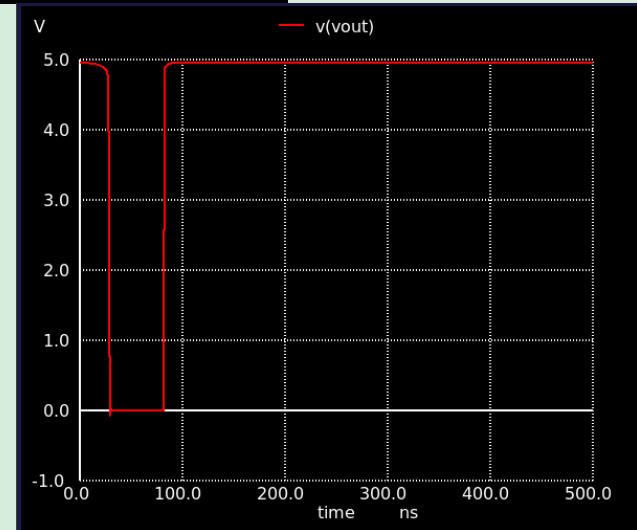



- Encontrar un  $V_{bias}$  adecuado
- Variar  $V_{bias}$  y  $V_{ref}$  en simulación dc.

- $V_{bias}$  entre 0.4 a 0.8

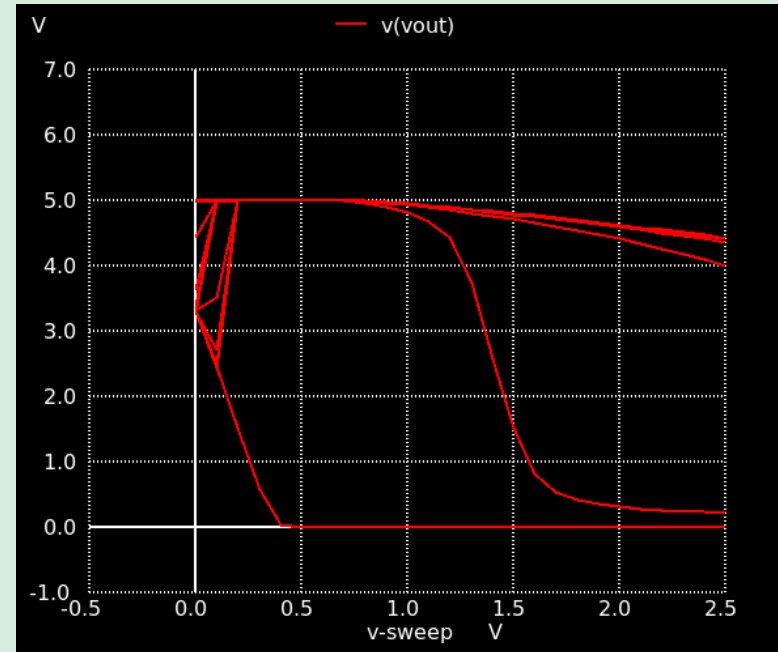


# Comparadores en uso:


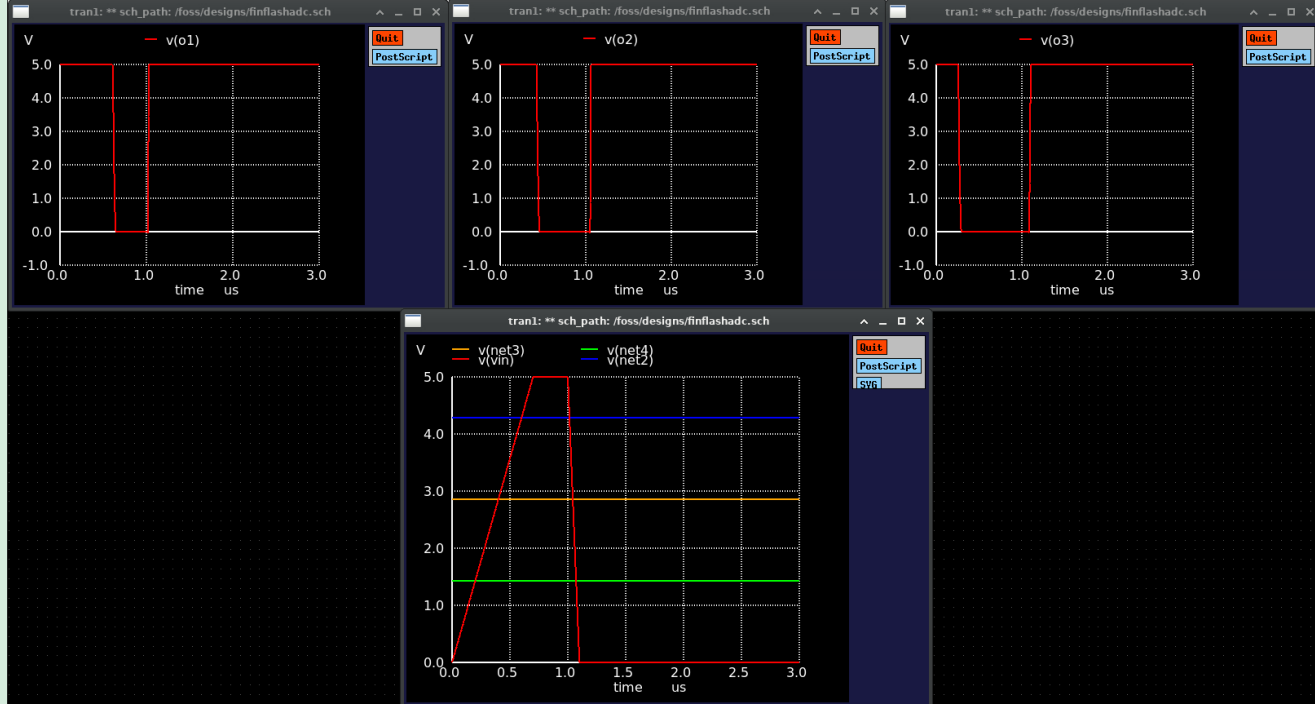
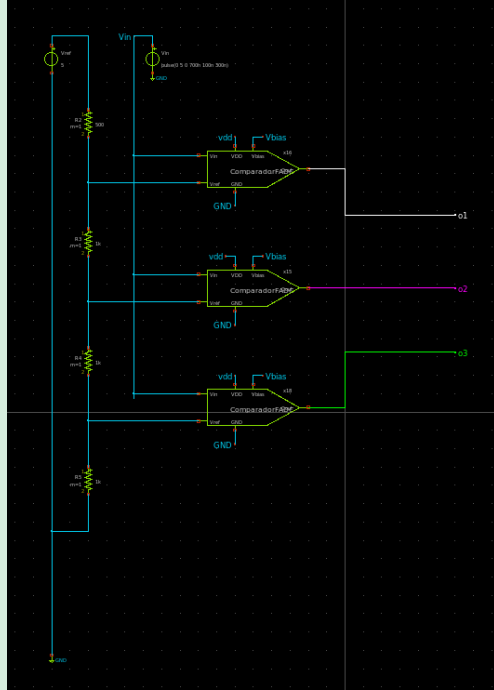


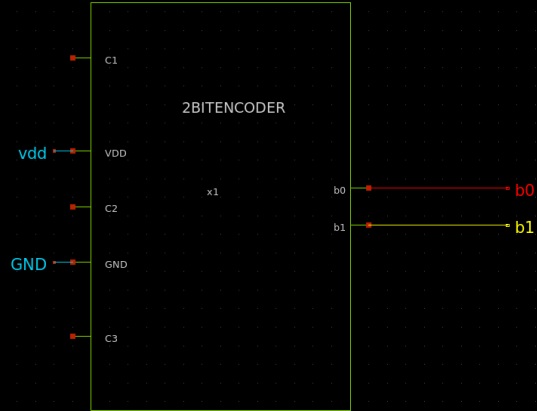

## Codificador de 2 bits:

- XNOR
- AND

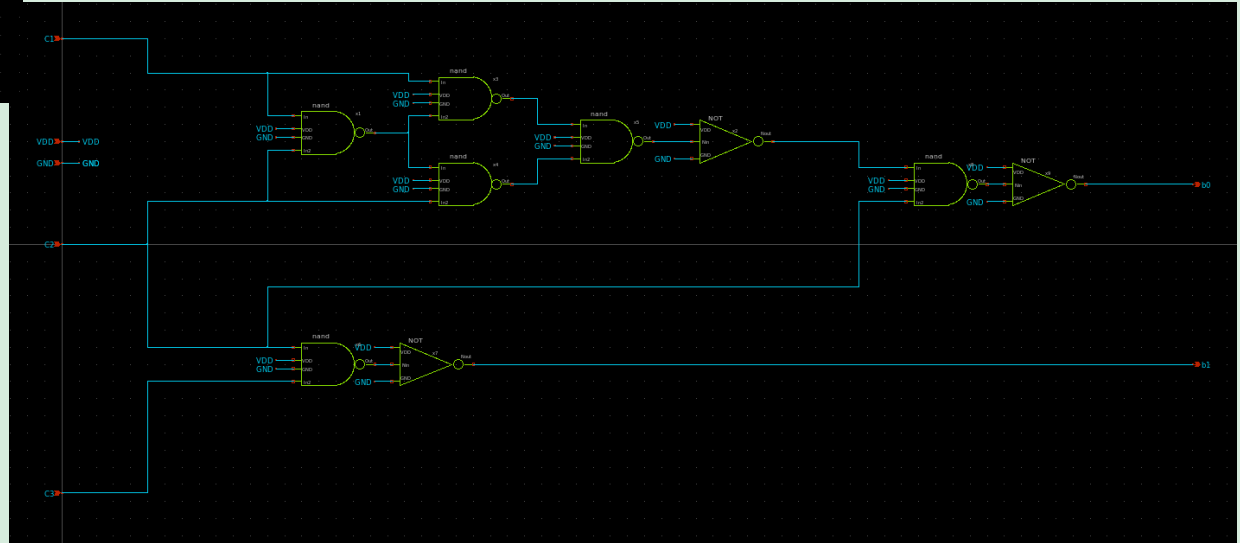


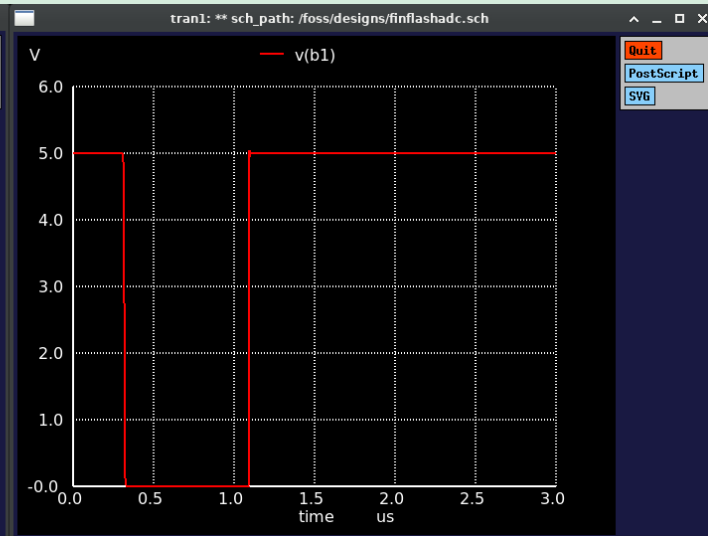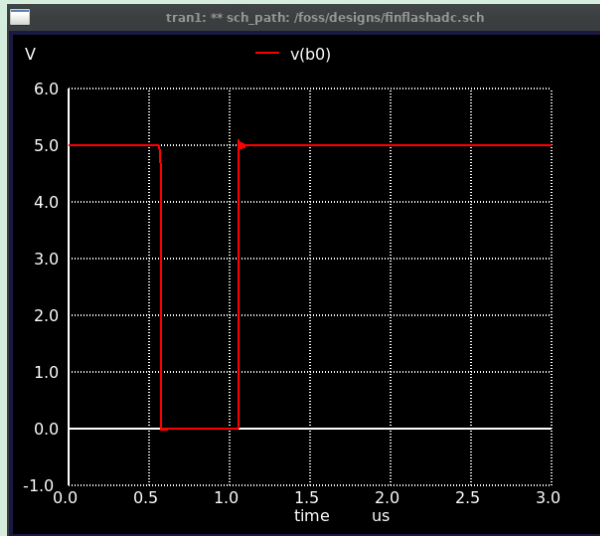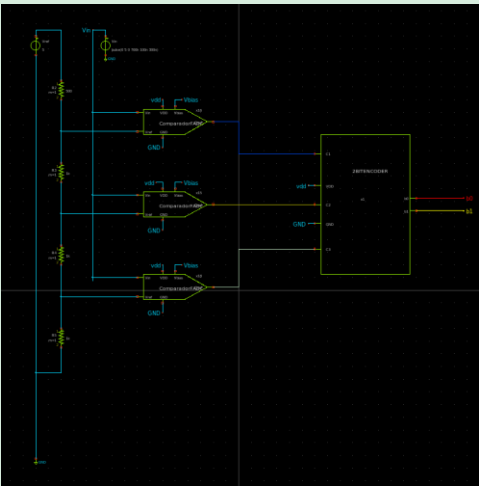








# Layout


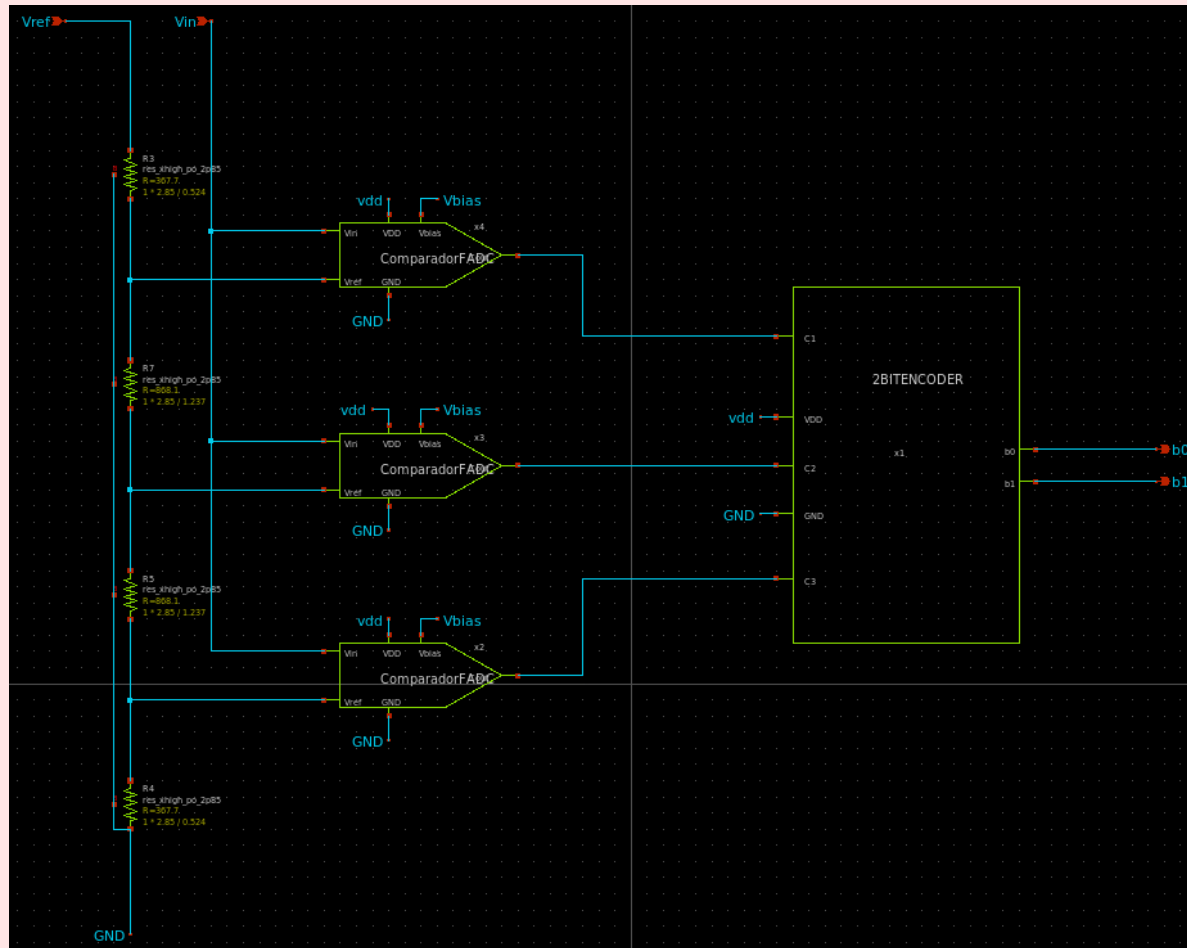


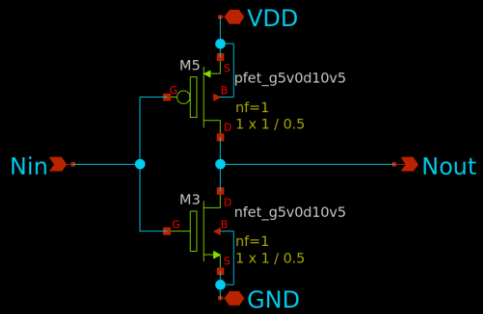


# Compuerta NOT

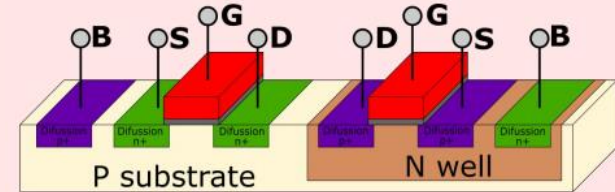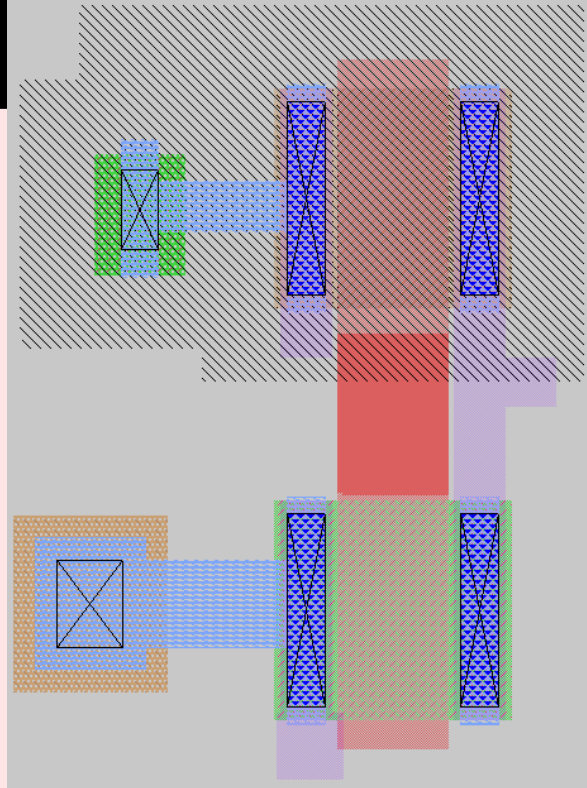


# Compuerta NAND

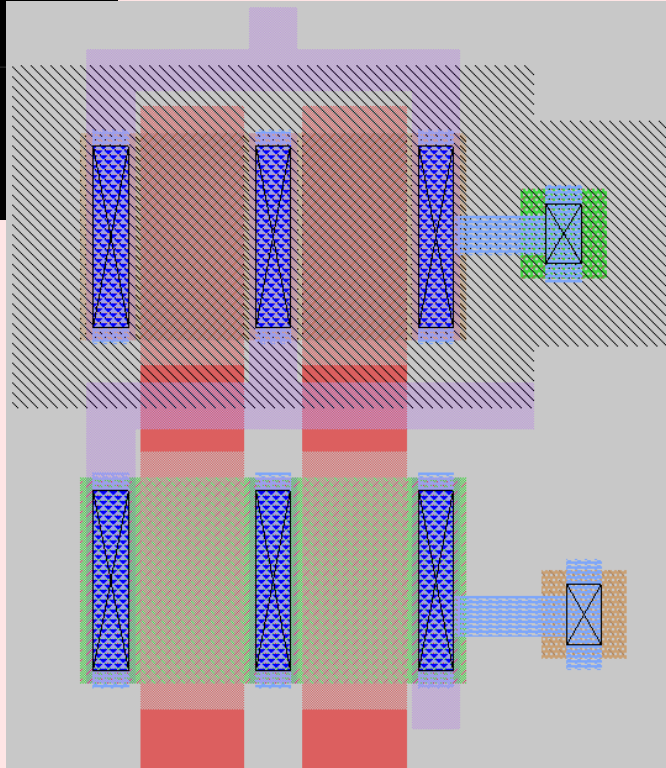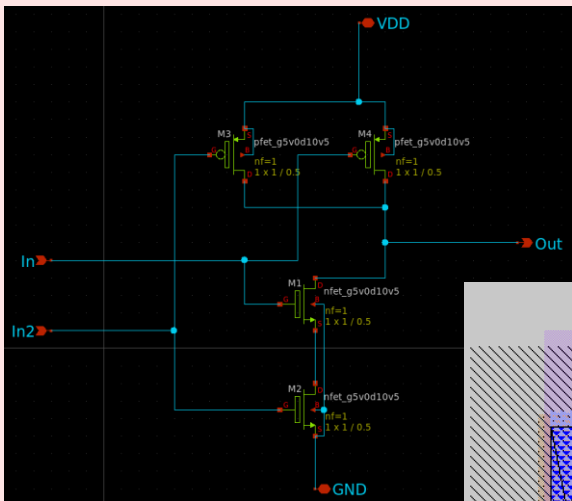


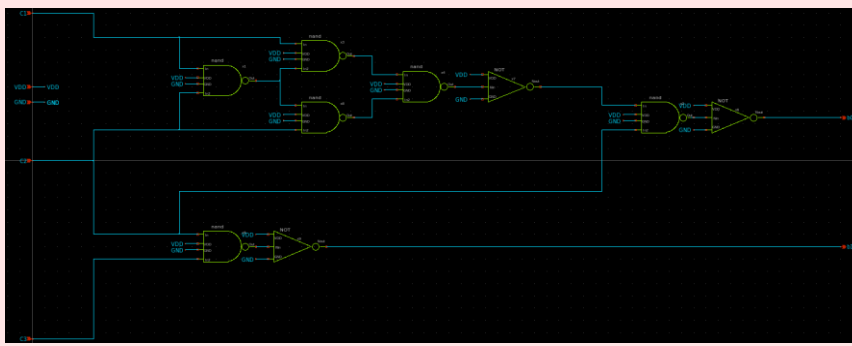

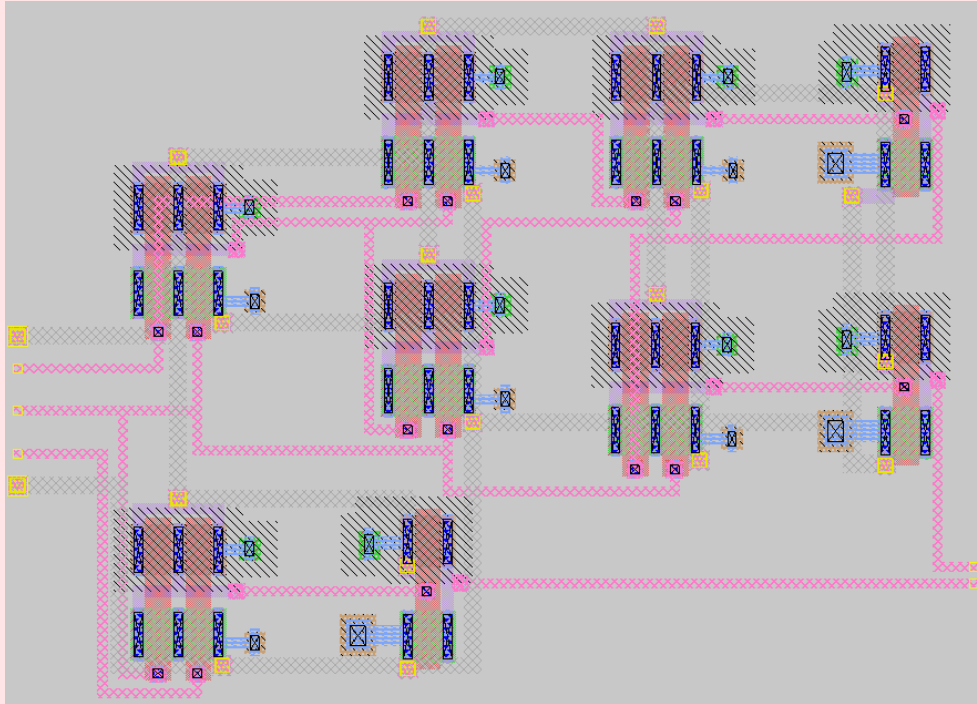
## Codificador de 2 bits

- Diseño mejorable  
Comparten Bulk.  
NAND y NOT Idénticos.






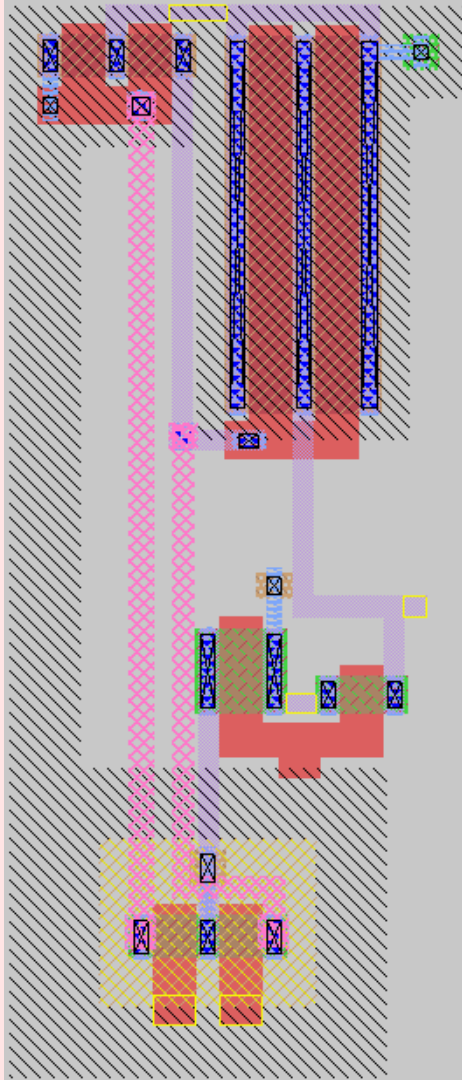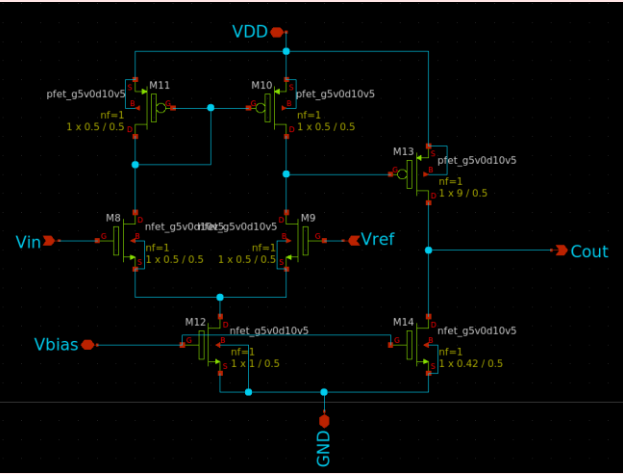
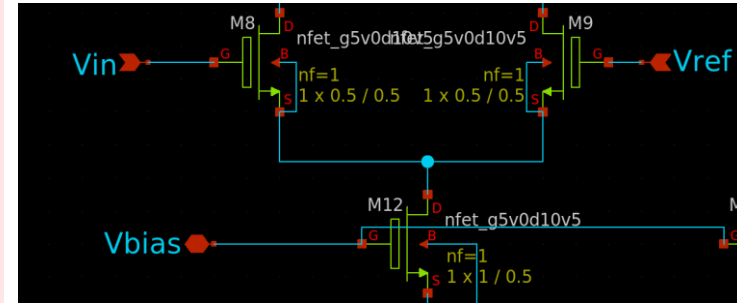
# Comparador


- Fingers.
- Aislación de transistores NFET.






# Esquemático FLASHADC

- Resistencias

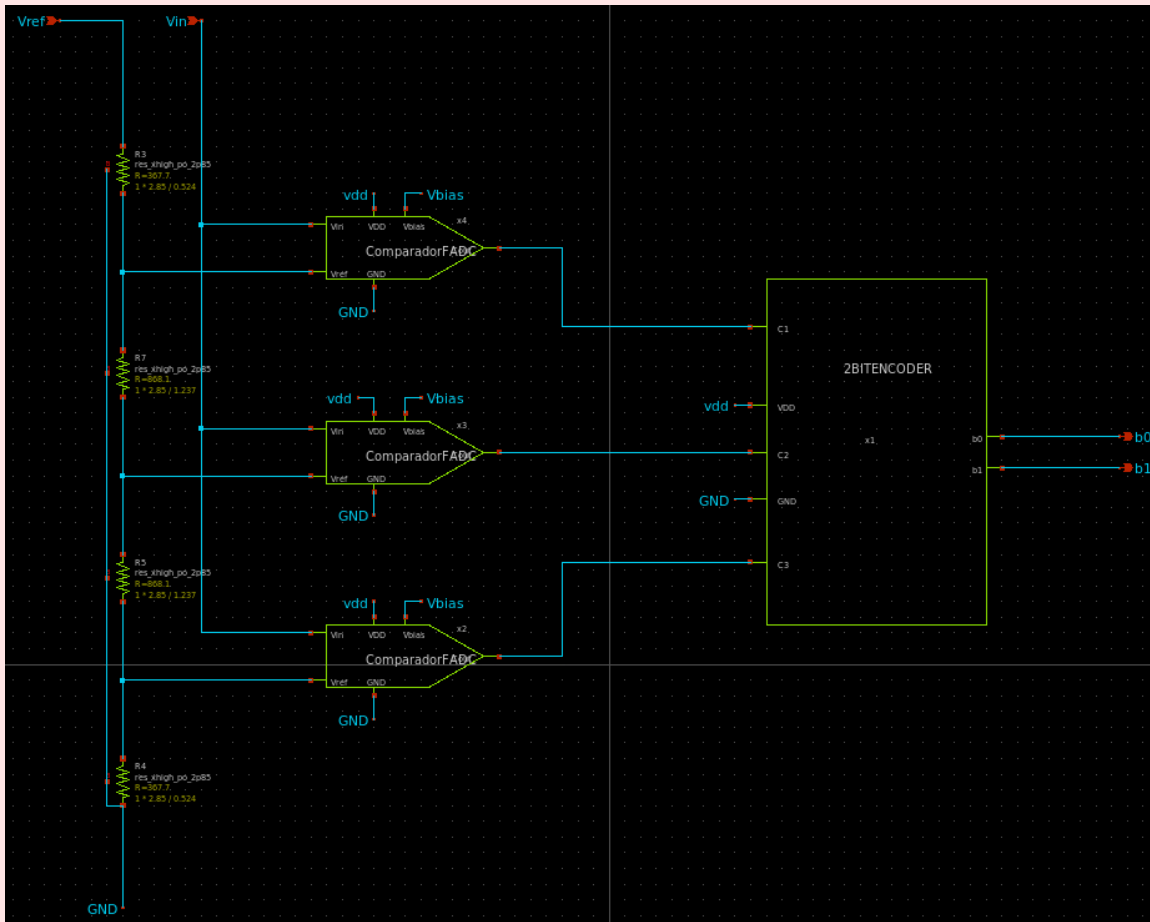

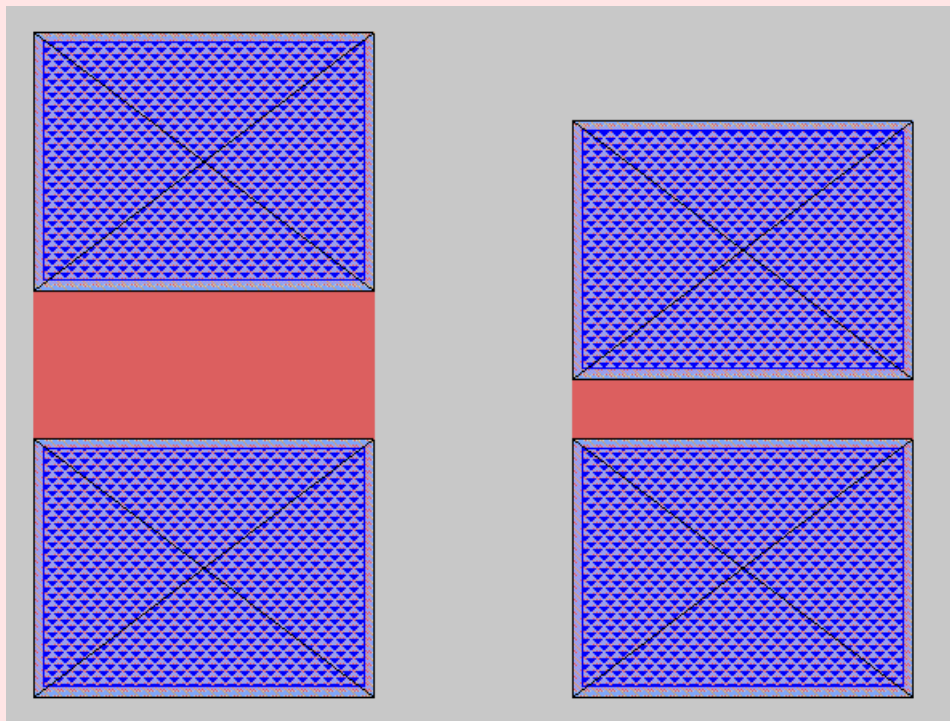


## Resistencias

$w = 2.85$

- 1000 ohm  $L = 1.237$
- 500 ohm  $L = 0.524$




# Layout FLASHADC


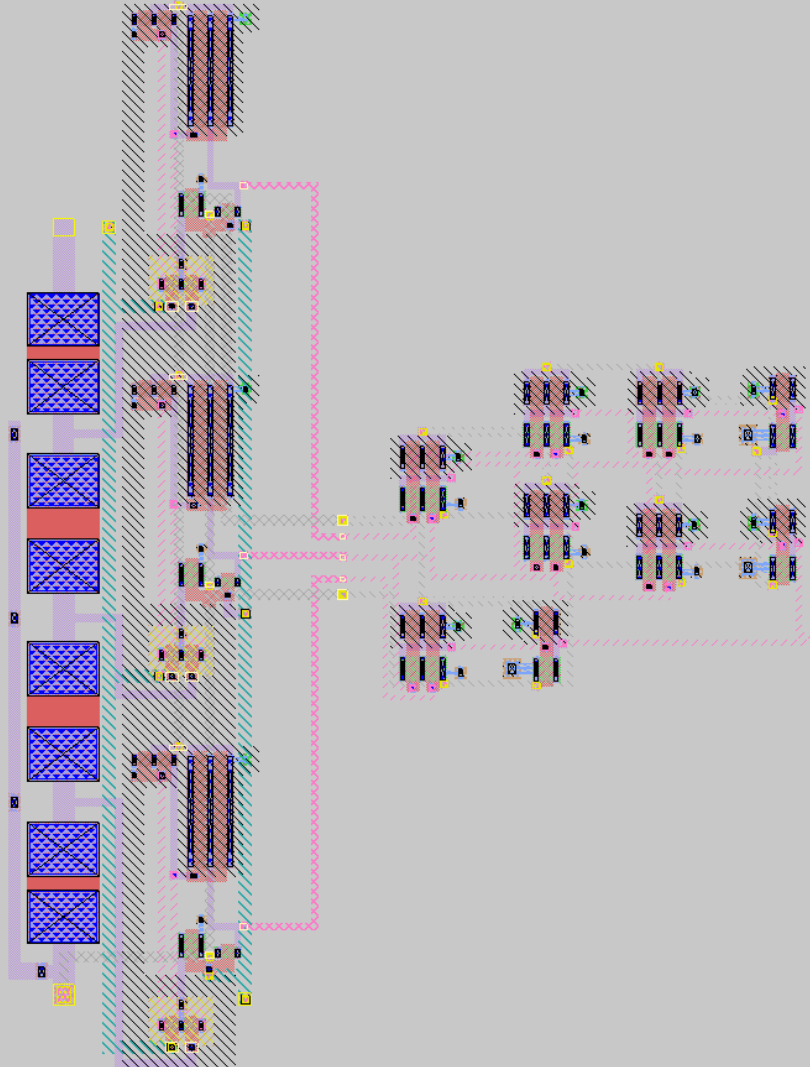


# **Simulación Post-Layout**



# Post Layout comparador

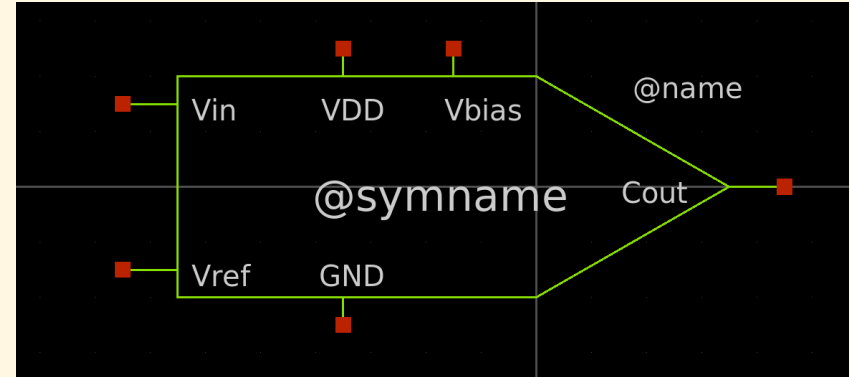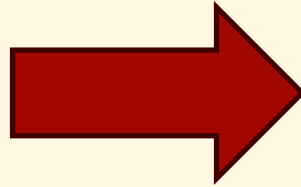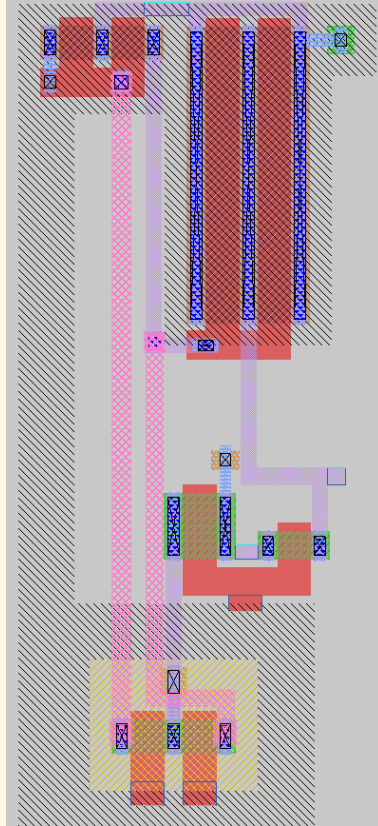

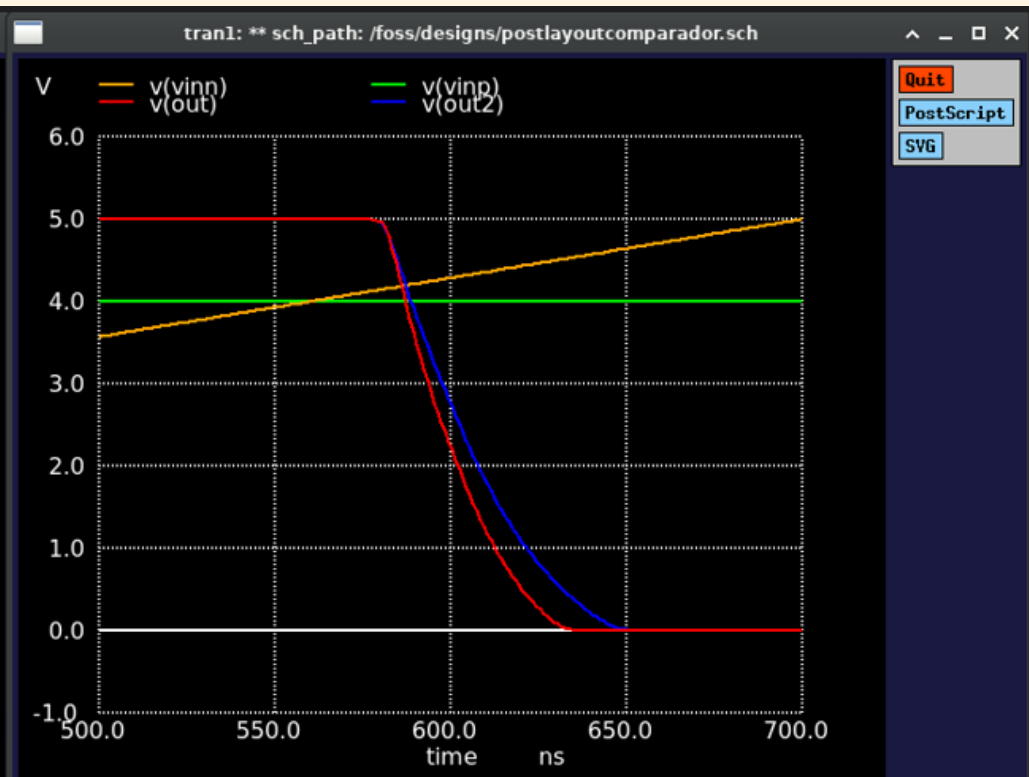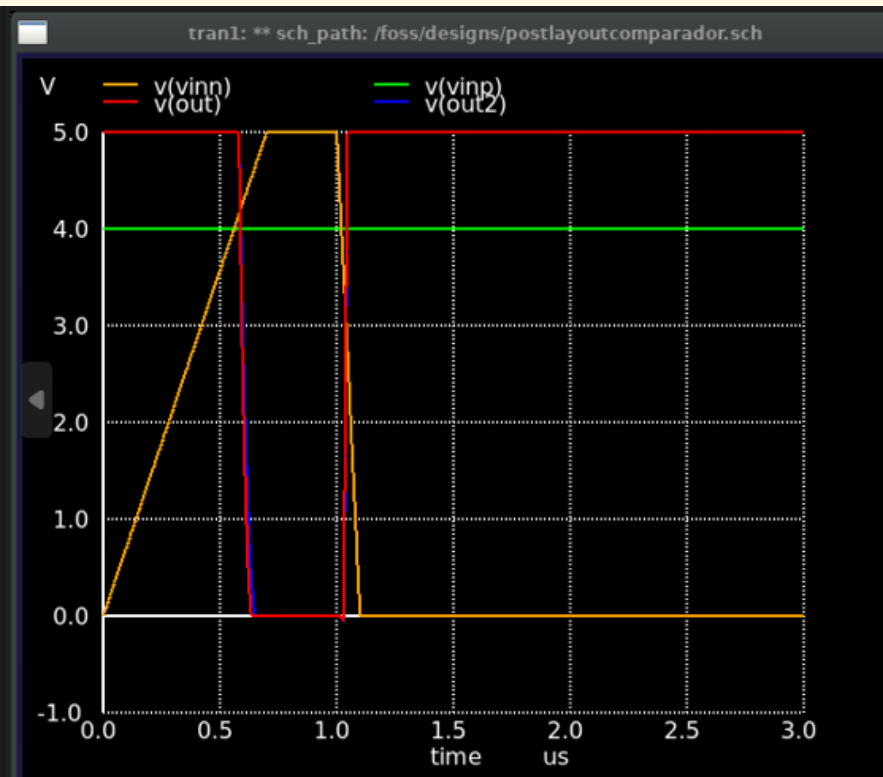



# Post Layout circuito completo

